

# Project Report

# CLAP SWITCH

# USING 555 TIMER IC

---

- Name : R.Thileeban
- Index No : 2023t01688
- Course : Analog and Digital Electronics

## 1. Introduction

The clap switch is a sound-activated circuit that triggers an electrical load (LED) when it detects a clap or sharp sound. This project utilizes the **NE555 timer IC** in monostable mode to create a reliable switching mechanism with adjustable timing.

### Key Features:

- **Input:** Electret microphone (GMI30 SP-2C64DB)
- **Core IC:** NE555 timer (monostable configuration)
- **Output:** LED indicator (expandable to relays)
- **Timing Range:** Adjustable via RC components (default: 11s)
- **Power Supply:** 5-12V DC

## 2. Circuit Design & Working Principle

### How It Works,

#### 1. Sound Detection:

- The electret mic (MIC1) picks up sound vibrations.
- A voltage spike is generated and fed to the **TRIGGER pin (Pin 2)** of the 555 IC.

#### 2. Monostable Operation:

- When triggered, the 555 output (**Pin 3**) goes **HIGH** for a fixed duration:


$$T=1.1\times R1\times C1=1.1\times 100k\Omega\times 100\mu F=11\text{ seconds}$$

- During this period, the **LED** lights up via current-limiting resistor **R2 (330Ω)**.

3. **Reset:**

- After 11 seconds, the output automatically turns **OFF** until the next clap.

PCB Schematic Diagram

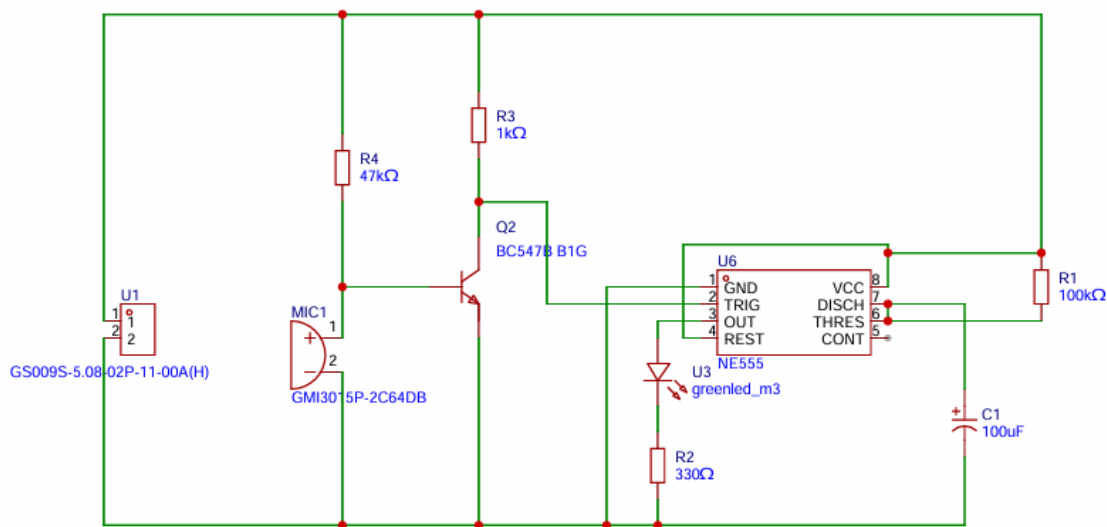



3. Clap Switch Component Summary

Component	Value/Specifications	Design Considerations
NE555 Timer IC (U3)	DIP-8 Package	Configure for monostable operation (Pin 2 trigger, Pin 3 output)
Terminal Block (U1)	GSO095-5.08-02P-11-00A(H)	5.08mm pitch, 2-pin for secure power input connections
Electret Mic (MIC1)	GMI30 SP-2C64DB (-44dB)	Requires 2-10V bias; R4 (47kΩ) sets sensitivity
Resistor (R1)	100kΩ, 1/4W	Critical for timing: Pulse width = $1.1 \times R1 \times C1$ ( $\approx 11s$ )




Component	Value/Specifications	Design Considerations
Capacitor (C1)	100μF, 16V Electrolytic	Low ESR type for stable timing; verify polarity
Resistor (R2)	330Ω, 1/4W	Limits LED current to ~9mA @5V ( $I_f = (V_{cc}-V_f)/R_2$ )
Transistor (Q2)	BC547B NPN (hFE:110-800)	Drives higher loads; base current $\geq (I_c/hFE)$
Resistor (R4)	47kΩ, 1/4W	Microphone bias resistor; adjust for trigger sensitivity
Resistor (R3)	1kΩ, 1/4W	Pull-up resistor for microphone signal conditioning
LED	5mm Green ( $V_f=2V$ , $I_f=20mA$ max)	Anode to R2 (330Ω); verify brightness at 9mA

## 4. Construction & Testing


### Simulation Results

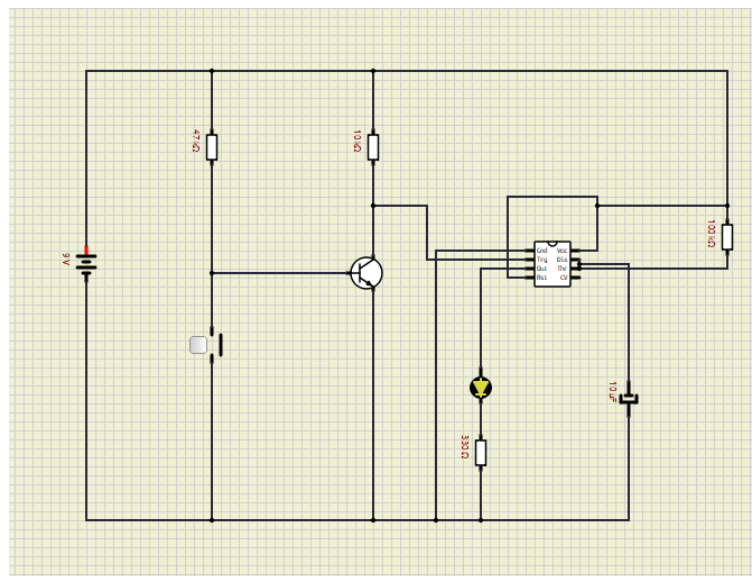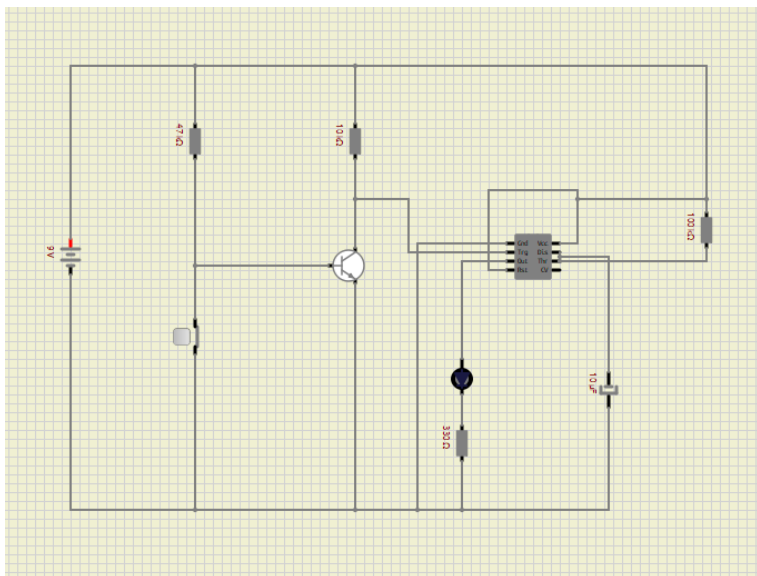



## Layout of PCB

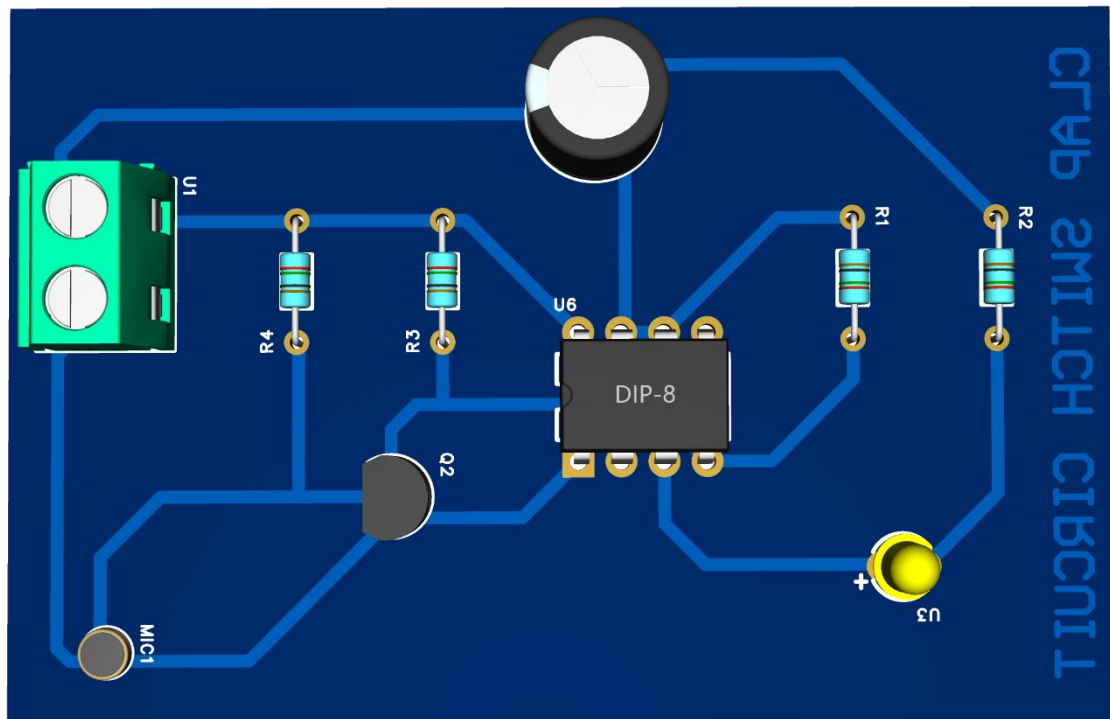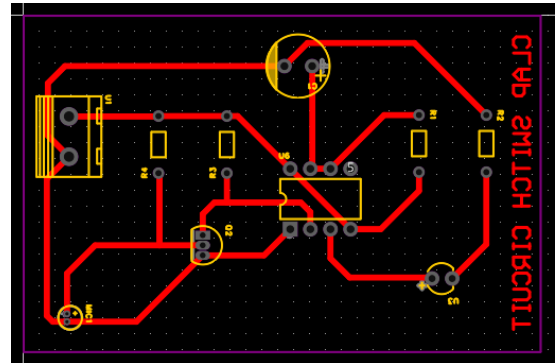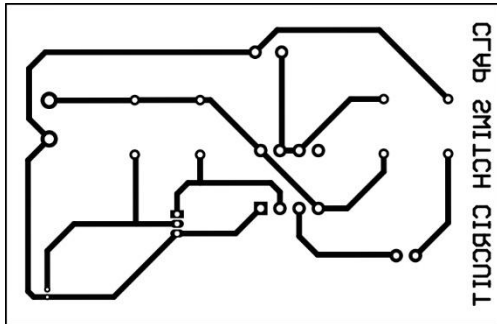

## Construction of PCB

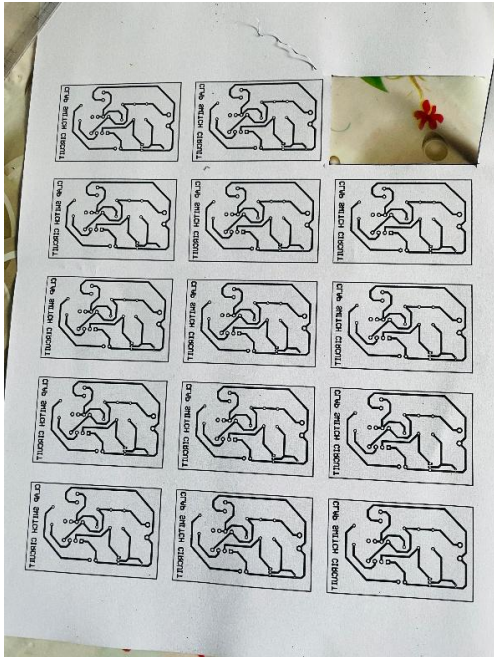



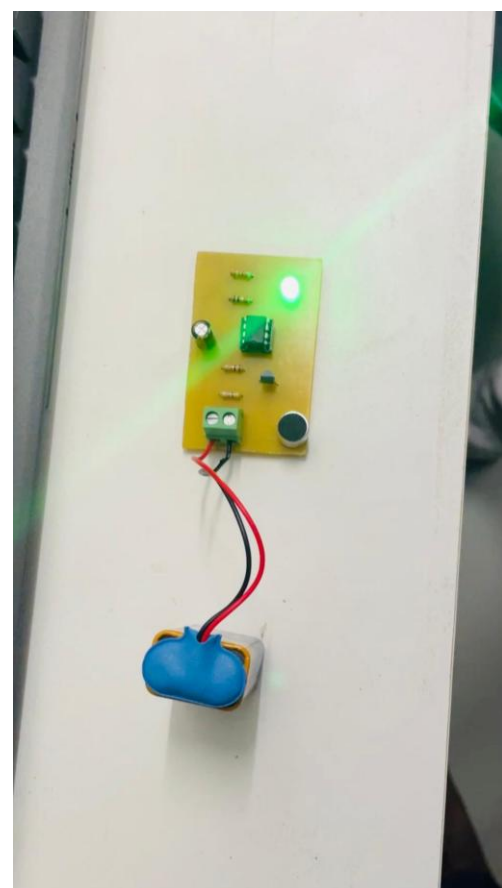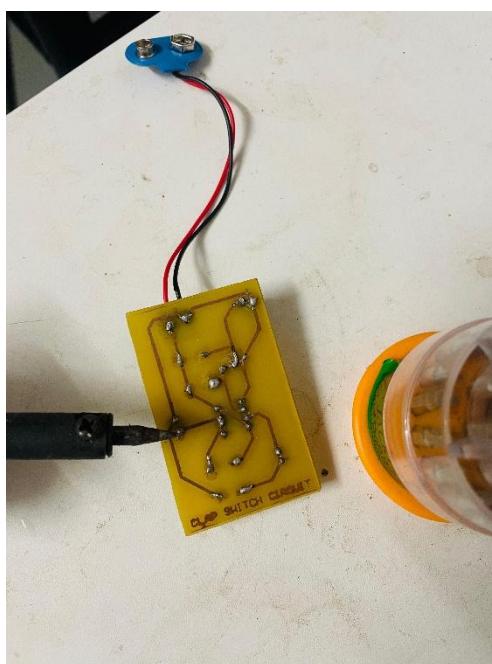

## 5. Applications & Improvements

### Practical Uses

- **Home Automation:** Control lights/fans with claps.
- **Assistive Tech:** Hands-free switches for disabled users.
- **Education:** Demo circuit for electronics labs.

## 6. Conclusion

The clap switch circuit successfully demonstrates sound-activated control using the 555 timer IC. With **11s output duration** and **reliable triggering**, it serves as a cost-effective solution for basic automation needs. Future improvements could include wireless integration or IoT compatibility.

### Appendices:

- Bill of Materials (BOM)
- Simulation Screenshots (Proteus/LTSpice)
- PCB Gerber Files